



## Analog Circuit Design

Peter D. Hiscocks

Professor Emeritus  
Department of Electrical and Computer Engineering  
Ryerson University

CEO  
Syscomp Electronic Design Limited

Email: [phiscock@ee.ryerson.ca](mailto:phiscock@ee.ryerson.ca)  
August 29, 2010

©Peter D. Hiscocks, 2010

*Understanding (an analog design) is like understanding a language. It doesn't take long to look at a schematic and know what it is all about if you know the language.*

Bob Dobkin, Vice President, Engineering, Maxim Integrated Circuits  
Designer of the LM118 Op Amp  
Quoted in [1]

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	Outline of the Material . . . . .	4
1.2	Converting Units of Measurement: A Systematic Method . . . . .	6
<b>2</b>	<b>Basic DC Circuits</b>	<b>7</b>
2.1	Voltage, Current and Resistance . . . . .	7
2.2	Electron Flow and Conventional Current: The Unlucky Guess of Benjamin Franklin . . . . .	7
2.3	Electronic Charge . . . . .	8
2.4	Voltage . . . . .	8
2.4.1	Example Voltages . . . . .	9
2.4.2	Voltmeter . . . . .	10
2.4.3	Voltage Standards . . . . .	10
2.5	Current . . . . .	10
2.5.1	Current Meter (Ammeter) . . . . .	11
2.5.2	Current Standards . . . . .	11
2.5.3	Example Currents . . . . .	11
2.5.4	Electron Conduction Physics [2] . . . . .	11
2.5.5	Velocity of Electron in a Vacuum Tube . . . . .	12
2.6	Resistance and Ohm's Law . . . . .	13
2.6.1	Example Resistances . . . . .	14
2.6.2	Resistance Standards . . . . .	15
2.6.3	Standard Values . . . . .	15
2.6.4	Conductivity . . . . .	15
2.6.5	Designing Resistors . . . . .	16
2.6.6	European Style Notation . . . . .	18
2.7	Ideal Voltage Source . . . . .	18
2.8	Ideal Current Source . . . . .	19
2.9	Kirchhoff's Voltage Law . . . . .	19
2.10	Kirchhoff's Current Law . . . . .	21
2.11	KVL, KCL and Circuit Analysis . . . . .	22
2.12	<i>Grounded</i> and <i>Floating</i> Components . . . . .	22
2.13	Resistors in Series . . . . .	23
2.14	Resistors in Parallel . . . . .	23
2.15	Resistor Networks . . . . .	24
2.16	Meters for Voltage, Current and Resistance . . . . .	24
2.16.1	Moving Coil Meter Movement . . . . .	24
2.16.2	Characterising an Unknown Meter Movement . . . . .	25
2.16.3	Moving Coil Voltmeter . . . . .	26
2.16.4	Moving Coil Ammeter . . . . .	27
2.16.5	Moving Coil Ohmmeter . . . . .	28
2.17	Practical Voltage Source . . . . .	29
2.18	Internal Resistance: Case Histories . . . . .	30
2.19	Practical Current Source . . . . .	33
2.20	Measuring Internal Resistance . . . . .	34
2.21	The <i>Load Line</i> . . . . .	35
2.22	Voltage and Current Source, Compared . . . . .	37

2.23	Power Dissipation . . . . .	39
2.24	Battery Tester . . . . .	40
2.25	The Capacitor . . . . .	41
2.25.1	Capacitor Construction . . . . .	42
2.25.2	Energy Storage in a Capacitor . . . . .	43
2.25.3	Energy Storage: Battery and Capacitor . . . . .	43
2.25.4	Common Misconception: Kirchoff's Current Law and The Capacitor . . . . .	44
2.26	The Capacitor: Time Domain . . . . .	44
2.26.1	Defective Circuit . . . . .	46
2.26.2	Energy Storage in a Capacitor: Reprise . . . . .	46
2.26.3	Application: Ramp Generator . . . . .	47
2.27	Capacitances in Series and Parallel . . . . .	48
2.28	The Inductor . . . . .	51
2.28.1	Voltage Induction . . . . .	51
2.28.2	Moving Magnet Induction . . . . .	51
2.28.3	Faraday's Law and Lenz's Law . . . . .	52
2.28.4	Inductance . . . . .	54
2.28.5	Energy Storage in an Inductor . . . . .	56
2.29	Inductance and Magnetism . . . . .	57
2.29.1	The Electric Circuit Analogy . . . . .	57
2.29.2	Reluctance . . . . .	58
2.29.3	Example: Variable Reluctance Sensor . . . . .	58
2.29.4	Deriving the Inductance . . . . .	59
2.29.5	Saturation . . . . .	60
2.29.6	Summary . . . . .	61
2.29.7	Solenoid Inductance on Ferrite Rod . . . . .	62
2.30	The <i>Amplifier</i> Concept . . . . .	62
2.31	Switches and Relays . . . . .	64
2.32	Exercises . . . . .	66
<b>3</b>	<b>Tools for Circuit Analysis: Part 1</b> . . . . .	<b>73</b>
3.1	Thevenin's Theorem . . . . .	73
3.2	Norton's Theorem . . . . .	75
3.3	The Voltage Divider . . . . .	75
3.4	Voltage Divider Design . . . . .	79
3.4.1	Exact Method . . . . .	79
3.4.2	Simple Method . . . . .	81
3.4.3	Graphical Method: Divider Design with Standard 5% Resistors . . . . .	84
3.4.4	Large Ratio Divider Shortcut . . . . .	85
3.4.5	Derivation of the Nomogram . . . . .	86
3.5	The Current Divider . . . . .	87
3.5.1	Current Divider Application: Meter Characterization . . . . .	87
3.6	The Superposition Theorem . . . . .	88
3.6.1	Applications . . . . .	88
3.6.2	Superposition and Power . . . . .	90
3.7	The Passive Adder . . . . .	91
3.8	The Wheatstone Bridge . . . . .	92
3.9	<i>Load Line</i> Application: Digital Logic Interface . . . . .	93

3.10	Component Tolerances . . . . .	99
3.11	Cumulative Tolerance . . . . .	99
3.12	Complex Cases: Spreadsheet to the Rescue . . . . .	101
3.13	Larger Problems . . . . .	103
3.14	Error Budget Analysis . . . . .	103
3.15	Exercises . . . . .	104
<b>4</b>	<b>Tools for Circuit Analysis: Part 2</b>	<b>108</b>
4.1	Alternating Current . . . . .	108
4.1.1	Waveforms in General . . . . .	108
4.1.2	Sinusoidal Waveforms . . . . .	109
4.2	Vector Notation and Sine Waves . . . . .	111
4.3	Reactance . . . . .	111
4.4	Complex Numbers . . . . .	112
4.5	Capacitive Reactance . . . . .	115
4.5.1	Capacitive Reactance in Vector Notation . . . . .	116
4.5.2	Example: Capacitive Reactance . . . . .	116
4.5.3	Example: Current in a Capacitor . . . . .	117
4.6	Inductive Reactance . . . . .	118
4.7	Reactance Calculators . . . . .	120
4.7.1	Reactance Chart . . . . .	120
4.7.2	Reactance Slide Rule . . . . .	122
4.7.3	Gnuplot Routine for Capacitive Reactance Chart . . . . .	122
4.8	RC Lowpass Network . . . . .	124
4.8.1	Example: Charging Capacitor . . . . .	125
4.9	RC Highpass Network . . . . .	127
4.10	Resonance, an Introduction . . . . .	128
4.11	Series Resonance . . . . .	129
4.11.1	Frequency Response . . . . .	130
4.11.2	Voltages and Currents in the Series Resonant Circuit . . . . .	131
4.12	Parallel Resonance . . . . .	131
4.12.1	Frequency Response . . . . .	132
4.13	Boing vs Thud: the Q Factor . . . . .	133
4.13.1	Defining Q Factor . . . . .	133
4.13.2	Q Factor and Energy Dissipation . . . . .	134
4.13.3	Q Factor and Voltage Magnification . . . . .	135
4.13.4	Q Factor, Bandwidth and Filter Shape . . . . .	135
4.14	Bandwidth of a Resonant Circuit . . . . .	136
4.14.1	Bandwidth and Q Factor . . . . .	137
4.15	The Compensated Attenuator . . . . .	139
4.16	The Ideal Transformer . . . . .	141
4.17	Impedance . . . . .	143
4.17.1	Impedance . . . . .	144
4.17.2	Using Impedance . . . . .	146
4.17.3	Impedance Matching . . . . .	147
4.18	Exercises . . . . .	148

<b>5</b>	<b>The Laplace Transform</b>	<b>149</b>
5.1	Overview	149
5.1.1	Laplace Notation as Shorthand	151
5.1.2	A Simple Example: Capacitor Charging Equation	151
5.1.3	Inductor Differential Equation	152
5.1.4	Capacitive Reactance	153
5.1.5	Summary	153
5.2	Transfer Function and Frequency Response	153
5.2.1	Transfer Function of Low Pass RC Filter	153
5.2.2	Magnitude and Phase of The Lowpass RC Filter	155
5.2.3	Measurement	156
5.2.4	Transfer Function of Low Pass LR Filter	157
5.2.5	Measurement	157
5.2.6	Transfer Function of a Second Order RLC Lowpass Filter	158
5.2.7	Magnitude and Phase of the Lowpass RLC Filter	160
5.2.8	Measurement	162
5.2.9	Transfer Function of the Two Stage (Second Order) RC Lowpass Filter	164
5.3	Time Domain Response	165
5.3.1	Computer Algebra: Using Maxima	165
5.3.2	Table of Transforms	168
5.3.3	Table of Transforms, Quadratic	168
5.3.4	Forcing Function: Unit Impulse	169
5.3.5	Forcing Function: Unit Step	170
5.3.6	Forcing Function: Unit Ramp	171
5.3.7	Unit Step and RC Lowpass	174
5.3.8	Unit Ramp and RC Lowpass	176
5.3.9	Capacitor with Initial Charge	180
5.3.10	LC Resonant Circuit	182
5.3.11	RLC Resonant Circuit	186
5.3.12	Two Stage (Second Order) Lowpass, Impulse Response	189
5.3.13	Comparing the Filters	191
5.4	Arbitrary Waveforms	192
5.4.1	Linearity Property	192
5.4.2	Time Shift Property	192
5.4.3	Example: Square Pulse	193
5.4.4	Example: Triangular Pulse	193
5.5	Appendices	194
5.5.1	Laplace Transform of Unit Impulse	194
5.5.2	Laplace Transform of the Unit Step	195
5.5.3	Gnuplot Magnitude and Phase Plotting Routines	196
5.5.4	Further Reading	198
5.6	Exercises	198
<b>6</b>	<b>The Semiconductor Diode</b>	<b>199</b>
6.1	Semiconductor Diode	199
6.2	Diode Logic OR Gate	200
6.3	Diode Logic AND Gate	201
6.4	Half Wave Rectifier	202

6.5	Full Wave Rectifier . . . . .	203
6.6	Diode Bridge Rectifier . . . . .	204
6.7	Diode Clamp . . . . .	205
6.8	Diode Clipping Circuit . . . . .	205
6.9	Bi-Directional Clipping . . . . .	206
6.10	The Flyback Diode . . . . .	207
6.11	Diode Types . . . . .	207
6.12	Exercises . . . . .	208
<b>7</b>	<b>The Zener Diode</b>	<b>212</b>
7.1	The Zener Diode . . . . .	212
7.2	Zener Regulator . . . . .	212
7.3	Zener Impedance . . . . .	214
7.4	Zener Regulator Amplifier . . . . .	215
7.5	Zener Current Drive . . . . .	216
7.6	Exercises . . . . .	217
<b>8</b>	<b>Active Devices</b>	<b>218</b>
8.1	The BJT: Bilateral Junction Transistor . . . . .	218
8.2	The JFET: Junction Field Effect Transistor . . . . .	220
8.3	The MOSFET: Metal Oxide Semiconductor Field Effect Transistor . . . . .	221
8.4	Application Circuit . . . . .	223
8.5	The MOSFET Switch . . . . .	224
8.6	The BJT Switch . . . . .	226
8.7	BJT Logic Devices . . . . .	228
8.8	The BJT Flip Flop . . . . .	230
8.9	Exercises . . . . .	231
<b>9</b>	<b>Motors and Generators</b>	<b>232</b>
9.1	DC Motor and Generator . . . . .	232
9.1.1	The Ideal DC Motor . . . . .	233
9.1.2	Real DC Generator Behaviour . . . . .	234
9.1.3	Speed Control . . . . .	234
9.1.4	Torque Control . . . . .	235
9.1.5	Alternatives . . . . .	235
<b>10</b>	<b>Negative Feedback</b>	<b>236</b>
10.1	Negative Feedback and Amplifiers . . . . .	238
10.2	Negative Feedback and the Operational Amplifier . . . . .	240
10.3	Minimizing Disturbances . . . . .	240
10.4	Negative Feedback Goes Bad . . . . .	242
10.5	Application: Temperature Controller . . . . .	244
10.6	Exercises . . . . .	247
<b>11</b>	<b>Reactance and Bode Plots</b>	<b>252</b>
11.1	Reactance Plot . . . . .	253
11.2	The Bode Plot . . . . .	256
11.3	Constant, Integrator and Differentiator Factors . . . . .	258
11.4	First Order Lead and Lag Factors . . . . .	259

11.5	First-order Lead . . . . .	259
11.6	First-order Lag . . . . .	261
11.7	Example: PID (Proportional, Integral, Differential) Controller . . . . .	262
11.8	Quadratic Factor . . . . .	264
11.9	Exercises . . . . .	266
<b>12</b>	<b>The Operational Amplifier: Basics</b>	<b>267</b>
12.1	Introduction . . . . .	267
12.2	The Op-Amp Comparator . . . . .	269
12.3	The Buffer . . . . .	270
12.4	The Non-Inverting Amplifier . . . . .	271
12.5	The Inverting Amplifier . . . . .	272
12.6	The Rules of Op-Amp Behaviour . . . . .	276
12.7	Single Supply Operation . . . . .	278
12.8	Exercises . . . . .	280
<b>13</b>	<b>The Operational Amplifier: Applications</b>	<b>285</b>
13.1	Miller Effect . . . . .	285
13.2	The Op-Amp Adder . . . . .	288
13.3	Non-Inverting Adder . . . . .	289
13.4	Sign Changer (Inverter) . . . . .	289
13.5	Switchable Sign Changer . . . . .	290
13.6	The Subtractor . . . . .	290
13.7	The Instrumentation Amplifier . . . . .	293
13.8	Universal Amplifier . . . . .	295
13.9	Current to Voltage Converter . . . . .	297
13.10	Integrator, Inverting . . . . .	298
13.11	Integrator, Non Inverting . . . . .	301
13.12	Differentiator . . . . .	303
13.13	Application: Spring-Mass Simulation . . . . .	306
13.14	Booster Stage . . . . .	308
13.15	Current Generator, Floating Load . . . . .	310
13.16	Current Generator, Grounded Load . . . . .	311
13.17	Charge Amplifier . . . . .	312
13.18	AC-Coupled Inverting Amplifier . . . . .	316
13.19	AC-Coupled Inverting Amplifier, Frequency Response . . . . .	319
13.20	AC-Coupled Non-Inverting Amplifier . . . . .	322
13.21	AC-Coupled Non-Inverting Amplifier, Frequency Response . . . . .	324
13.22	AC-Coupled Amplifier, Miscellaneous Issues (Advanced) . . . . .	327
13.23	Input and Output Resistance . . . . .	329
13.24	Summary of Amplifier Circuits . . . . .	336
13.25	Exercises . . . . .	340
<b>14</b>	<b>The Schmitt Trigger</b>	<b>353</b>
14.1	Introduction . . . . .	353
14.2	Schmitt Trigger, Inverting . . . . .	354
14.3	Schmitt Trigger, Non-Inverting . . . . .	356
14.4	Exercises . . . . .	358



<b>15 Power Supplies</b>	<b>360</b>
15.1 AC Power Distribution . . . . .	361
15.2 Power Supply Configuration . . . . .	363
15.3 Rectifier-Filter Configurations . . . . .	365
15.4 Series and Shunt Voltage Regulators . . . . .	372
15.5 Feedback Voltage Regulator . . . . .	374
15.6 Three-terminal Linear Regulator . . . . .	376
15.7 The AC Adaptor . . . . .	378
15.8 Switching Regulator . . . . .	380
15.9 Switching Regulator, Design Example . . . . .	393
15.10 Charge Pump . . . . .	399
15.11 Voltage Multiplier . . . . .	402
15.12 Transformer Design . . . . .	403
15.13 Transformer Design Parameters . . . . .	408
15.14 Application: Transformer Isolated Interface . . . . .	410
15.15 Example: Transformer Design . . . . .	412
15.16 Summary of Power Supply Design . . . . .	417
15.17 Appendix: The Transformer Voltage Equation . . . . .	420
15.18 Appendix: Transformer Power Equation . . . . .	422
15.19 Appendix: Wire Table . . . . .	426
15.20 Appendix: Calculating the Effective (RMS) Value of a Waveform . . . . .	427
15.21 Exercises . . . . .	432
<b>16 Precision Rectifiers</b>	<b>439</b>
16.1 Precision Diode . . . . .	441
16.2 Precision Half-Wave Rectifier . . . . .	443
16.3 Precision Full-Wave Rectifier . . . . .	444
16.4 Full-Wave Meter Driver . . . . .	447
16.5 Phase-Sensitive Rectifier . . . . .	448
16.6 RMS Conversion . . . . .	449
16.6.1 Obvious Implementation . . . . .	449
16.6.2 The Implicit Method . . . . .	449
16.7 Thermal Method . . . . .	450
16.8 Peak Detector . . . . .	451
16.8.1 Improved Peak Detector . . . . .	451
16.9 Sample-Hold Circuit . . . . .	453
16.10 Exercises . . . . .	455
<b>17 Active Filters</b>	<b>456</b>
17.0.1 Introduction . . . . .	456
17.0.2 Applications . . . . .	456
17.0.3 Function . . . . .	457
17.0.4 Symbols . . . . .	457
17.0.5 Order . . . . .	458
17.0.6 Shape . . . . .	458
17.0.7 Sensitivity . . . . .	459
17.0.8 Implementation . . . . .	460
17.0.9 Roadmap to the Section . . . . .	460

17.1	First-Order Filters . . . . .	461
17.1.1	First Order Active Filters . . . . .	463
17.2	Example: A Simple Bandpass Filter . . . . .	464
17.3	Second-Order Low-Pass Filter . . . . .	466
17.3.1	Transfer Function of the First Order Cascade . . . . .	467
17.4	Second-Order Band-Pass Filter . . . . .	472
17.5	Second-Order High-Pass Filter . . . . .	474
17.6	Second-Order Band-Reject (Notch) Filter . . . . .	476
17.7	Summary, Second-Order Filters . . . . .	479
17.8	The <i>Bronzite</i> Circuit . . . . .	480
17.9	The <i>Sallen-Key</i> Lowpass Circuit . . . . .	482
17.10	The <i>Sallen-Key</i> Highpass Circuit . . . . .	487
17.11	The <i>State Variable</i> Circuit . . . . .	488
17.12	Notch Filter Circuits . . . . .	492
17.13	State Variable Notch . . . . .	492
17.14	The Twin-Tee Network . . . . .	493
17.14.1	Tuneable Passive Notch Filter . . . . .	495
17.15	Higher Order Filters . . . . .	495
17.16	The <i>Butterworth</i> Characteristic . . . . .	496
17.17	Designing A Butterworth Filter . . . . .	496
17.18	The <i>Chebyshev</i> Characteristic . . . . .	499
17.19	The <i>Bessel</i> Characteristic . . . . .	506
17.20	Plotting High-Order Filter Characteristics . . . . .	507
17.21	First-Order Transient Response . . . . .	509
17.22	Second-Order Transient Response . . . . .	509
17.23	Filter Tables . . . . .	511
17.24	Design Method Overview . . . . .	514
17.25	Appendix: The Complex Frequency Plane . . . . .	515
17.25.1	Poles and Zeros . . . . .	515
17.25.2	The Second-Order Lowpass Filter, Normalized . . . . .	516
17.25.3	The Complex Frequency Plane . . . . .	518
17.25.4	Zeros at Infinity . . . . .	518
17.25.5	The <i>Membrane</i> Model . . . . .	519
17.25.6	Amplitude and Phase Response from the Complex Frequency Plane . . . . .	520
17.25.7	Generalizing the Amplitude and Phase Response . . . . .	522
17.25.8	Example: The Highpass Filter . . . . .	522
17.26	Summary of Common Pole-Zero Configurations . . . . .	524
17.27	Exercises . . . . .	527
<b>18</b>	<b>The Zoo: Unusual Circuits</b> . . . . .	<b>535</b>
18.1	NIC: Negative Impedance Converter . . . . .	535
18.2	Capacitance Multiplier . . . . .	537
18.3	Howland Current Generator . . . . .	539
18.4	Simple Gyrator . . . . .	541
18.4.1	Transient Analysis: A Reality Check . . . . .	542
18.4.2	Assessment . . . . .	543
18.5	Improved Gyrator . . . . .	543
18.6	FDNR: Frequency Dependent Negative Resistance . . . . .	546

18.6.1	Application	546
18.6.2	Circuit	547
18.7	Circulator	548
18.8	Exercises	550
<b>19</b>	<b>Phase Shift Networks</b>	<b>554</b>
19.1	Passive Network Phase Shifter	554
19.1.1	Improved Phase Shifter	554
19.1.2	Analysis of the All-Pass Network	554
19.1.3	Bode Plots	555
19.2	Op-Amp Phase Shifter	556
19.3	Wideband Phase Shifter	557
19.4	Exercises	559
<b>20</b>	<b>Oscillators</b>	<b>560</b>
20.0.1	Oscillator as Negative Feedback System	560
20.0.2	Oscillation and Negative Resistance	560
20.0.3	Comparator Driven Oscillator	560
20.0.4	Simulation Note	560
20.1	Phase Shift Oscillator	561
20.1.1	A Design Example	561
20.2	Wien Bridge Oscillator	563
20.2.1	References	565
20.3	Wien Bridge Oscillator, Amplitude Stabilization	565
20.4	Quadrature Oscillator	567
20.5	Three-Phase Oscillator	570
20.5.1	Analysis	570
20.6	Schmitt Trigger Astable	572
20.7	Function Generator	574
20.8	Exercises	576
<b>21</b>	<b>The Non-Ideal Operational Amplifier</b>	<b>580</b>
21.1	Finite Gain	581
21.2	Bias Current	582
21.3	Offset Voltage	584
21.4	Power Supply Rejection Ratio	587
21.5	Common Mode Rejection Ratio	590
21.6	Output Voltage and Current Limit	593
21.7	Output Resistance	594
21.8	Slew Rate	596
21.9	Noise and Bandwidth	600
21.10	Exercises	600
<b>22</b>	<b>Operational Amplifier Noise</b>	<b>609</b>
22.1	Resistor Noise	612
22.2	Noise Spectrum	614
22.3	Effective Noise Bandwidth	616
22.4	Op-amp Noise	617
22.5	Noise Gain	621

22.6	Noise Example: Voltage Follower . . . . .	622
22.7	Noise Example: Inverter . . . . .	624
22.8	Noise Formulae . . . . .	627
22.9	Exercises . . . . .	630
<b>23</b>	<b>Operational Amplifier Frequency Response</b>	<b>632</b>
23.1	Introduction . . . . .	632
23.2	Gain-Bandwidth . . . . .	633
23.3	Maximum Useful Frequency . . . . .	635
23.4	Single Pole Response . . . . .	637
23.5	Quadratic Response . . . . .	640
23.6	Exercises . . . . .	644
<b>24</b>	<b>Stability</b>	<b>645</b>
24.1	Introduction . . . . .	645
24.2	Decoupling . . . . .	646
24.3	Phase Margin and Stability . . . . .	647
24.4	The <i>Intercept</i> Rule . . . . .	649
24.5	Reduced Noise Gain . . . . .	651
24.6	Output Buffer Stage . . . . .	654
24.7	Input Capacitance . . . . .	656
24.8	Frequency Compensation: The Lag-Lead Network . . . . .	657
24.9	Capacitive Loading . . . . .	661
24.10	Exercises . . . . .	667
<b>25</b>	<b>Digital to Analog Conversion</b>	<b>669</b>
25.1	D/A Specifications . . . . .	670
25.2	Weighted Resistor D/A . . . . .	672
25.3	R-2R D/A: Current Steering Mode . . . . .	673
25.4	R-2R D/A: Voltage Switching Mode . . . . .	674
25.5	The <i>MDAC</i> : Multiplying Digital to Analog Converter . . . . .	676
25.6	MDAC Applications . . . . .	678
25.7	Pulse Width Modulation . . . . .	681
25.8	Exercises . . . . .	685
<b>26</b>	<b>Analog to Digital Conversion</b>	<b>686</b>
26.1	Signal to Noise Ratio . . . . .	686
26.2	Aliasing . . . . .	688
26.3	Feedback Converters . . . . .	689
26.4	Single Slope Technique . . . . .	691
26.5	Dual Slope Technique . . . . .	694
26.6	Sigma-Delta Oversampling Converter . . . . .	696
26.7	Voltage to Frequency Converter . . . . .	700
26.8	Exercises . . . . .	704

<b>27 Opto-Electronic Devices</b>	<b>708</b>
27.1 Introduction . . . . .	708
27.2 Light Emitting Diode . . . . .	709
27.3 Photodiode . . . . .	710
27.4 Photoresistive Cell . . . . .	712
27.5 Phototransistor . . . . .	713
27.6 Optocoupler . . . . .	714
27.7 Exercises . . . . .	715
<b>28 Cooling</b>	<b>719</b>
28.1 Thermal Circuits . . . . .	720
28.2 The Derating Curve . . . . .	721
28.3 Designing a Heatsink: Calculating Thermal Resistance . . . . .	722
28.4 Heatsink Area . . . . .	724
28.5 Thermal Capacitance . . . . .	725
28.6 Fan Cooling . . . . .	727
28.7 Power Dissipation in an Operational Amplifier . . . . .	729
28.7.1 Example . . . . .	730
28.7.2 Solution . . . . .	730
28.8 Exercises . . . . .	732
<b>29 The Single Stage BJT Amplifier</b>	<b>734</b>
29.1 Introduction . . . . .	734
29.2 The Diode Model . . . . .	735
29.3 BJT Nomenclature . . . . .	736
29.4 The Current Generator Model . . . . .	737
29.5 Base Current Control . . . . .	738
29.6 Base Voltage Control . . . . .	741
29.7 The Ramp Generator . . . . .	743
29.8 Emitter Current Control . . . . .	745
29.9 The Ramp Generator: Improved . . . . .	746
29.10 Reflecting Resistance . . . . .	750
29.11 Collector Resistance . . . . .	752
29.12 Temperature and Base-Emitter Voltage . . . . .	757
29.13 Temperature and Leakage Current . . . . .	760
29.14 DC BJT Circuits and Equations . . . . .	763
29.15 Bias Stability and Beta . . . . .	768
29.16 Emitter Incremental Resistance and BJT Transconductance . . . . .	769
29.17 Transconductance and Distortion . . . . .	772
29.18 The Common Emitter Amplifier . . . . .	773
29.19 The Common Emitter Amplifier, Analysis . . . . .	775
29.20 Common Emitter Amplifier with Emitter Resistance . . . . .	782
29.21 Common Emitter Amplifier with Enhancements . . . . .	786
29.22 The Common Emitter Amplifier, Base Current Drive . . . . .	793
29.23 Common-Emitter Amplifier with Collector-Base Feedback . . . . .	796
29.24 A Catalogue of Common Emitter Configurations . . . . .	801
29.25 Summary: Common-Emitter Equations . . . . .	804
29.26 The Common Collector (Emitter Follower) Amplifier . . . . .	805

29.27	Summary: Emitter Follower Equations . . . . .	811
29.28	The Emitter Follower as a Negative Feedback System . . . . .	812
29.29	Emitter Follower Design Example . . . . .	815
29.30	The Common Base Amplifier . . . . .	822
29.31	Summary: Common-Base Equations . . . . .	826
29.32	The Inverted Transistor . . . . .	827
29.33	Noise in the BJT . . . . .	828
29.34	BJT Noise Current and Other Considerations . . . . .	829
29.35	Problems . . . . .	830
29.36	Appendix: Determining the Transistor Parameters . . . . .	830
29.37	Appendix: A discussion of Models . . . . .	836
29.38	Appendix: Base-Emitter Voltage Function of Temperature . . . . .	837
29.39	Appendix: BJT Datasheet . . . . .	843
<b>30</b>	<b>BJT-Compounds</b>	<b>847</b>
30.1	The Darlington Pair . . . . .	847
30.2	The Sziklai Pair . . . . .	849
30.3	The Current Source . . . . .	851
30.4	Discrete Component Sink . . . . .	851
30.5	The Current Mirror . . . . .	853
30.6	Discrete Component Current Mirror . . . . .	855
30.7	Multiple-Output Current Mirror . . . . .	858
30.8	The Wilson Current Mirror . . . . .	860
30.9	Appendix: Output Resistance of Common-Emitter Stage with Emitter Degeneration . . . . .	862
30.10	Appendix: Mirror Emitter Degeneration Resistors . . . . .	863
30.11	Appendix: Wilson Mirror Output Resistance . . . . .	864
30.12	The Cascode Pair . . . . .	866
30.13	Folded Cascode Pair . . . . .	870
30.14	The Differential Pair . . . . .	870
	30.14.1 BJT Differential Amplifier, Transfer Characteristic . . . . .	871
30.15	Enhanced Differential Pair . . . . .	878
	30.15.1 Darlington-Differential . . . . .	882
	30.15.2 Cascode-Differential . . . . .	883
	30.15.3 Differential Stage Coupling . . . . .	883
	30.15.4 Appendix: Diff Amp Transfer Characteristic . . . . .	884
	30.15.5 The <i>tanh</i> Function . . . . .	886
	30.15.6 Appendix: Dual Stage Differential Amplifier Bias and Gain . . . . .	886
30.16	Series-Shunt Feedback Pair . . . . .	889
30.17	An Operational Amplifier Design . . . . .	894
30.18	Exercises . . . . .	902
<b>31</b>	<b>JFET Characteristics and Applications</b>	<b>913</b>
31.1	Constant Current Diode . . . . .	913
31.2	Transfer Characteristic . . . . .	915
31.3	The JFET Switch . . . . .	918
	31.3.1 Opto-Isolated JFET Switch . . . . .	920
31.4	The JFET Amplifier . . . . .	920
	31.4.1 Playing to the Strengths of the JFET . . . . .	920

31.4.2	BJT and JFET Op-Amps . . . . .	921
31.4.3	Transconductance of the BJT . . . . .	921
31.4.4	Transconductance of the JFET . . . . .	922
31.4.5	Transresistance of the JFET . . . . .	923
31.5	The Source Follower . . . . .	924
31.5.1	Notes on the Source Follower Circuit . . . . .	924
31.5.2	The JFET Small Signal Model . . . . .	925
31.5.3	Voltage Gain of the Source Follower . . . . .	925
31.5.4	Summary: Source Follower Equations . . . . .	927
31.6	JFET Common Source Amplifier and Common Gate Amplifier . . . . .	928
31.7	JFET Compound Amplifiers . . . . .	928
31.7.1	JFET Differential Amplifier . . . . .	928
31.7.2	Oscilloscope Buffer Amplifier . . . . .	928
31.8	Appendix: Interpreting the JFET Datasheet . . . . .	930
31.9	Exercises . . . . .	932
<b>32</b>	<b>The MOSFET Family</b>	<b>934</b>
32.1	Linear Applications of the MOSFET Transistor . . . . .	934
32.2	MOSFET Transfer Characteristic . . . . .	934
32.3	The Enhancement Mode MOSFET . . . . .	935
32.4	The Depletion Mode MOSFET . . . . .	936
32.5	DC Coupled Source Follower . . . . .	936
32.5.1	Biasing the Follower . . . . .	936
32.5.2	Voltage Gain of the Follower . . . . .	937
32.5.3	Output Resistance of the Follower . . . . .	938
32.6	Biasing the Enhancement Mode MOSFET: AC Coupled Follower . . . . .	940
32.7	Applying MOSFETs in Linear Applications . . . . .	941
32.8	Vertical and Lateral Format MOSFETs . . . . .	941
32.9	MOSFET Power Amplifier Output Stage . . . . .	942
32.9.1	Drive Current and Voltage . . . . .	942
32.9.2	Thermal Stability and Crossover Distortion . . . . .	943
32.9.3	Output Voltage Swing . . . . .	944
32.9.4	Bandwidth . . . . .	944
32.10	Exercises . . . . .	945
<b>33</b>	<b>CMOS Analog Switch and Applications</b>	<b>946</b>
33.1	Applications . . . . .	947
33.1.1	Mixer Input Select . . . . .	947
33.1.2	Switched Gain Amplifier . . . . .	948
33.1.3	Logic Circuits . . . . .	949
<b>34</b>	<b>Interference</b>	<b>950</b>
34.1	Scope of the Problem . . . . .	950
34.2	The Mechanism of Interference . . . . .	952
34.3	The Source . . . . .	952
34.4	The Coupling Mechanism . . . . .	952
34.5	Conductive Coupling . . . . .	953
34.5.1	Implications for PC Board Layout . . . . .	954

34.6	Electric Field Coupling . . . . .	954
34.6.1	Electric-Field Detection . . . . .	955
34.6.2	Electric-Field Shielding . . . . .	955
34.6.3	Demonstration: Electric Field Pickup . . . . .	956
34.6.4	Demonstration: Reducing Electric Field Pickup by Lowering Impedance . . . . .	957
34.6.5	Demonstration: Reducing Electric Field Pickup by Shielding . . . . .	957
34.7	Magnetic Field Coupling . . . . .	957
34.7.1	Magnetic Field Identification . . . . .	959
34.7.2	Voltage in the Conductor . . . . .	959
34.7.3	Demonstration: Magnetic Field Pickup . . . . .	961
34.7.4	Magnetic Field Shielding . . . . .	961
34.8	Spectrum of Pulse Waveform . . . . .	964
34.8.1	Square Wave Spectrum . . . . .	964
34.8.2	Trapezoidal Wave Spectrum . . . . .	965
34.8.3	The Bode Approximation . . . . .	965
34.8.4	Derivation: Spectrum of Trapezoidal Waveform . . . . .	966
34.9	Components of The Hidden Schematic . . . . .	967
34.9.1	Wiring Resistance . . . . .	968
34.9.2	Resistance of Printed Wiring Traces . . . . .	969
34.9.3	Wiring Inductance . . . . .	971
34.9.4	Inductance of a Printed Wiring Trace . . . . .	972
34.9.5	Power Supply Inductance and The Bypass Capacitor . . . . .	973
34.9.6	Parasitic Inductance in Capacitors . . . . .	974
34.9.7	Capacitor Resonance . . . . .	976
34.9.8	Broadbanding the Bypass Capacitor . . . . .	976
34.10	Common Mode and Differential Signals . . . . .	976
34.10.1	Rejection of Ground Conductor Noise . . . . .	977
34.10.2	Differential Amplifier Enhancements . . . . .	978
34.10.3	Guarding . . . . .	979
34.10.4	Bifilar Choke . . . . .	979
34.11	EMC: Electromagnetic Compliance . . . . .	980
34.11.1	EMI from Differential and Common Mode Currents . . . . .	981
34.11.2	Common Mode Current, EMI, and the Bifilar Choke . . . . .	982
34.11.3	Differential Drive and Common-Mode EMI Current . . . . .	983
34.11.4	Evaluating EMC . . . . .	983
34.12	Electromagnetic Field Coupling . . . . .	984
34.13	Measurement Technique . . . . .	985
34.13.1	Single Lead Connection . . . . .	986
34.13.2	Twin Lead Connection . . . . .	986
34.13.3	Coaxial Cable Connection . . . . .	988
34.13.4	$\times 10$ Probe Connection . . . . .	988
34.13.5	Active Probe Connection . . . . .	989
34.14	Printed Wiring Board Layout . . . . .	989
34.14.1	A/D Converter Layout and Grounding . . . . .	990
34.14.2	Ground Plane and the A/D Converter . . . . .	993
34.15	Case Histories: Solved . . . . .	993
34.16	Exercises . . . . .	994



<b>35 Beyond the Op-Amp</b>	<b>997</b>
35.1 Introduction	997
35.1.1 Voltage-Mode and Current Mode Circuits	997
35.1.2 Why is the Op-Amp so Popular?	997
35.1.3 Why Consider Other Amplifier Architectures?	998
35.1.4 Other Types of Amplifiers	998
35.2 The Current Conveyor	999
35.2.1 Example	999
35.2.2 Internal Circuit Operation	999
35.2.3 Application	1000
35.3 The <i>Current Feedback</i> Amplifier	1001
35.3.1 Basic Operation	1002
35.3.2 Gain Analysis	1003
35.3.3 Loop Gain	1003
35.3.4 Maximum Frequency of Operation	1004
35.3.5 Transresistance Equivalent Circuit	1004
35.3.6 Slew Rate	1005
35.3.7 References	1005
35.4 The <i>Norton</i> Amplifier	1006
35.4.1 Norton Internals	1006
35.4.2 Equivalent Circuit	1006
35.4.3 Bias for AC Amplification	1007
35.4.4 AC Amplifier	1007
35.4.5 Discussion	1007
35.5 Operational Transconductance Amplifier	1008
35.5.1 Internal Circuitry	1008
35.5.2 OTA Application: Voltage Controlled Amplifier	1009
35.6 The Comparator Device	1010
35.7 Instrumentation Amplifier	1011
35.8 Fully Differential Amplifier	1013
35.8.1 Differential and Common-Mode Signals	1013
35.8.2 Differential Signalling	1014
35.8.3 Internal Circuit	1015
35.8.4 Example Design: Transient Capture	1015
35.8.5 Rules of Ideal Behaviour	1016
35.8.6 Differential Gain Analysis	1017
35.8.7 Common-Mode Analysis	1018
35.8.8 Design Example: Single-Ended to Differential Converter	1019
35.8.9 Selecting Resistor Value	1021
35.9 Autozero Amplifier	1022
35.10 Chopper Amplifier	1024
35.11 Composite Amplifier	1027
35.12 Exercises	1028

<b>36 Multiplier</b>	<b>1033</b>
36.1 Introduction	1033
36.2 MDAC: Multiplying Digital to Analog Converter	1035
36.3 Duty Cycle (Pulse Width-Height) Multiplier	1035
36.4 Transconductance Multiplier	1037
36.5 Exercises	1042
<b>37 Complete Systems</b>	<b>1044</b>
37.1 Equation Solver	1044
37.2 DC Motor Controller	1046
37.2.1 Real DC Motor Behaviour	1046
37.2.2 The Control System	1047
37.2.3 Control System Equations	1047
37.2.4 Electronic Circuit	1049
37.2.5 Results	1050
37.3 Sumo Competition Robot	1051
37.3.1 Robot Behaviour	1051
37.3.2 Robot Power Supply	1052
37.3.3 Motor Driver Circuit	1053
37.3.4 Edge Detection Subsystem	1054
37.3.5 Object Detector and Speed Control	1055
37.3.6 Object Detector Circuit	1056
37.4 The Synchro Resolver	1058
37.4.1 Resolver Interface, Design	1060
37.4.2 Resolver Interface, Circuit Diagram	1061
37.5 The Linear Variable Differential Transformer	1063
37.6 Analogue Correlation Techniques	1064
37.6.1 Correlation Overview	1064
37.6.2 The Correlation Time Delay	1064
37.6.3 Correlation and Signal Processing	1065
37.6.4 Correlation and the Phase Sensitive Rectifier	1067
37.7 Barometer Interface	1068
37.7.1 The Pressure Sensor	1068
37.7.2 Sensor Specifications	1069
37.7.3 Pressure Sensor Equivalent Circuit	1069
37.7.4 Barometer Resolution and Dynamic Range	1070
37.7.5 Transfer Function	1071
37.7.6 Designing the Circuit	1072
37.7.7 Complete Circuit	1074
37.7.8 Reliability of the Design	1075
37.7.9 Circuit Analysis for Component Tolerance and Temperature Drift	1076
37.7.10 Calibration	1077
37.8 Exercises	1079
37.9 Design Exercises	1081
37.10 Extended Design Exercise: Telescope Heater	1085
<b>Bibliography and References</b>	<b>1092</b>